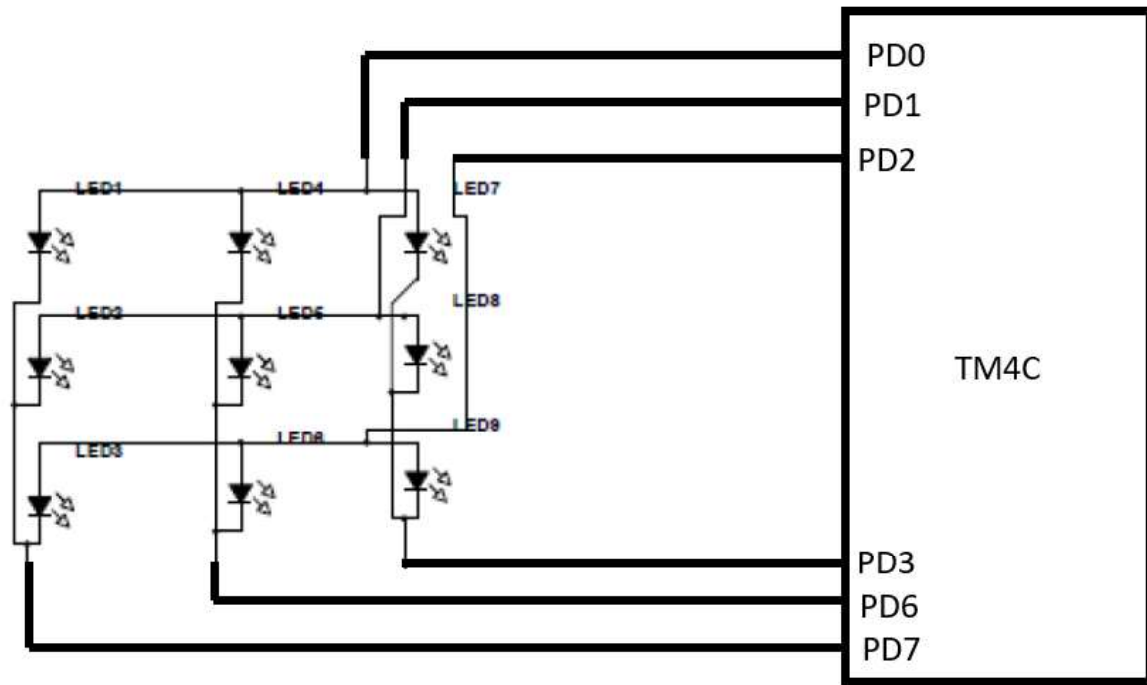


## Lab 2: Learning GPIO port interface in TIVA $\mu$ C

### (3x3 LED with TIVA)

Circuit Diagram:



**Exercise 2:** Using diode logic provide digital high and low to the corresponding GPIO pins to achieve the following in the circuit shown above

- (i) Toggle the LEDs on and off in row or column, using on-board switch SW1
- (ii) Toggle the direction of lighting using SW2